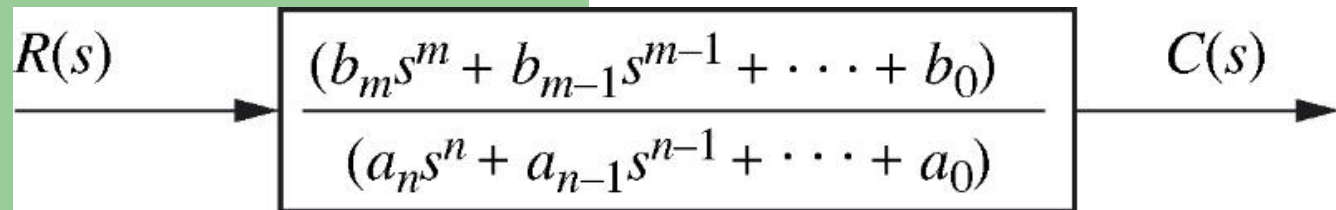


# Modeling in the Frequency Domain



System & Control Engineering Lab.  
School of Mechanical Engineering

# CHAPTER OBJECTIVES

- Review the Laplace transform
- Learn how to find a mathematical model, called a transfer function, for linear, time-invariant electrical, mechanical, and electromechanical systems
- Learn how to linearize a nonlinear system in order to find the transfer function

# Control System Model



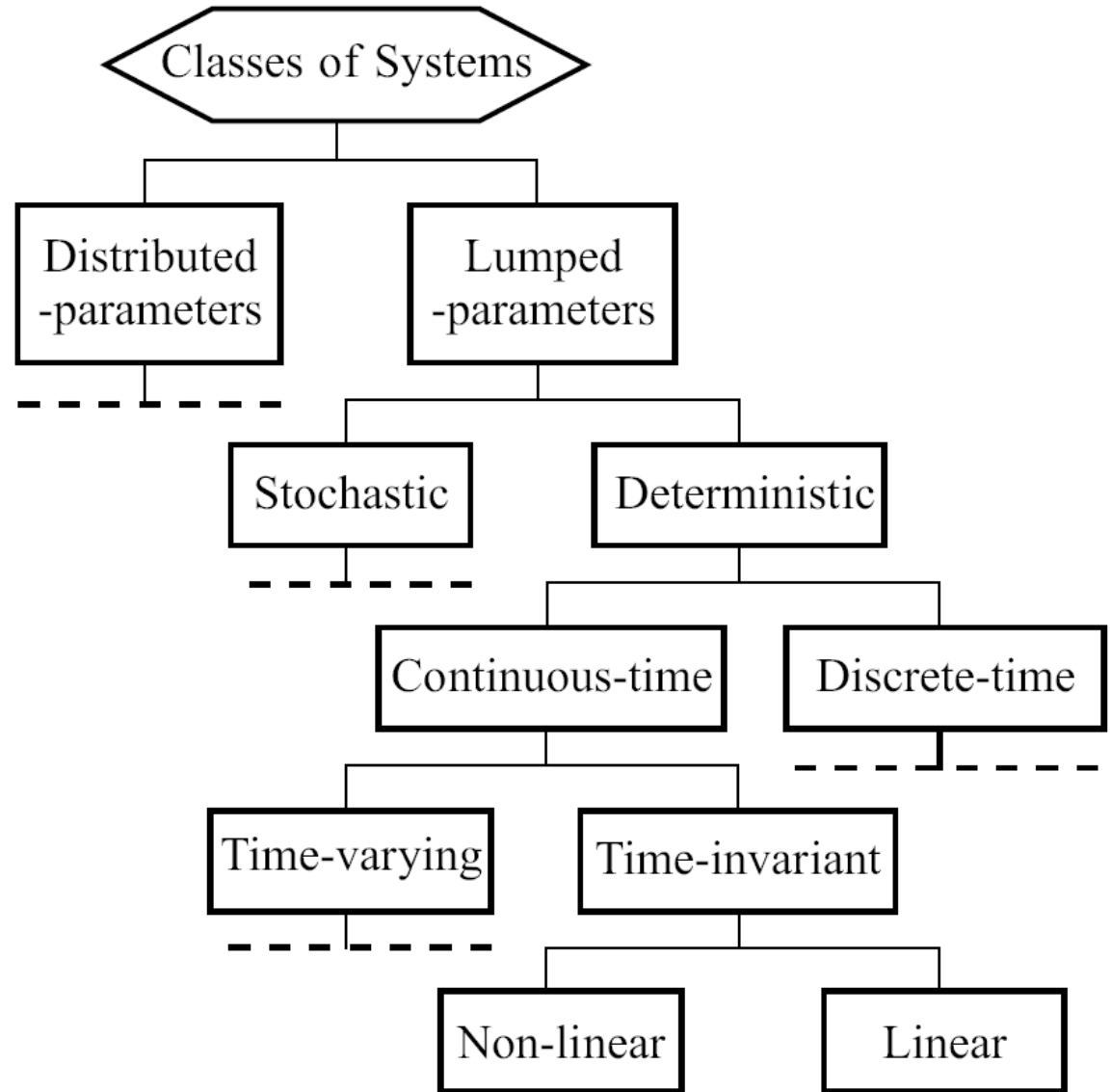


Fig. 2.1 Major classes of system equations

# Block Diagram

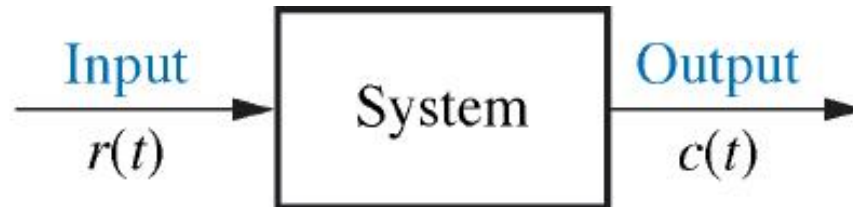

(a)

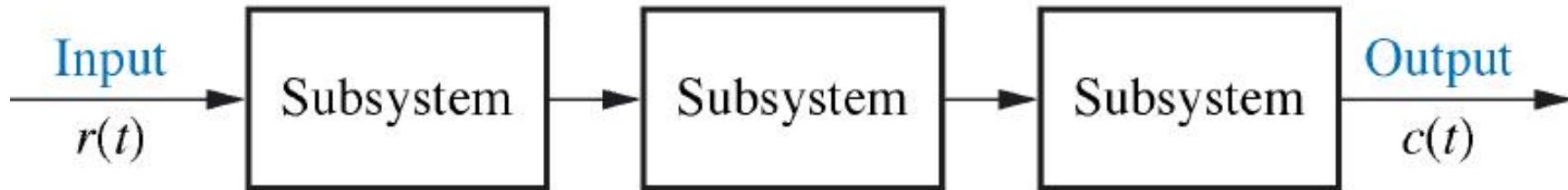

(b)

Note: The input,  $r(t)$ , stands for *reference input*.  
The output,  $c(t)$ , stands for *controlled variable*.

# LAPLACE TRANSFORM REVIEW

$$\mathcal{L}[f(t)] = F(s) = \int_{0-}^{\infty} f(t)e^{-st} dt \quad (2.1)$$

TABLE 2.1 Laplace transform table


Item no.	$f(t)$	$F(s)$
1.	$\delta(t)$	1
2.	$u(t)$	$\frac{1}{s}$
3.	$tu(t)$	$\frac{1}{s^2}$
4.	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5.	$e^{-at} u(t)$	$\frac{1}{s+a}$
6.	$\sin \omega t u(t)$	$\frac{\omega}{s^2 + \omega^2}$
7.	$\cos \omega t u(t)$	$\frac{s}{s^2 + \omega^2}$

# LAPLACE TRANSFORM REVIEW

**TABLE 2.2** Laplace transform theorems

Item no.	Theorem	Name
1.	$\mathcal{L}[f(t)] = F(s) = \int_{0-}^{\infty} f(t)e^{-st} dt$	Definition
2.	$\mathcal{L}[kf(t)] = kF(s)$	Linearity theorem
3.	$\mathcal{L}[f_1(t) + f_2(t)] = F_1(s) + F_2(s)$	Linearity theorem
4.	$\mathcal{L}[e^{-at} f(t)] = F(s + a)$	Frequency shift theorem
5.	$\mathcal{L}[f(t - T)] = e^{-sT} F(s)$	Time shift theorem
6.	$\mathcal{L}[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$	Scaling theorem
7.	$\mathcal{L}\left[\frac{df}{dt}\right] = sF(s) - f(0-)$	Differentiation theorem
8.	$\mathcal{L}\left[\frac{d^2f}{dt^2}\right] = s^2F(s) - sf(0-) - f'(0-)$	Differentiation theorem
9.	$\mathcal{L}\left[\frac{d^nf}{dt^n}\right] = s^n F(s) - \sum_{k=1}^n s^{n-k} f^{(k-1)}(0-)$	Differentiation theorem
10.	$\mathcal{L}\left[\int_{0-}^1 f(\tau) d\tau\right] = \frac{F(s)}{s}$	Integration theorem
11.	$f(\infty) = \lim_{s \rightarrow 0} sF(s)$	Final value theorem <sup>1</sup>
12.	$f(0+) = \lim_{s \rightarrow \infty} sF(s)$	Initial value theorem <sup>2</sup>

# TRANSFER FUNCTIONS

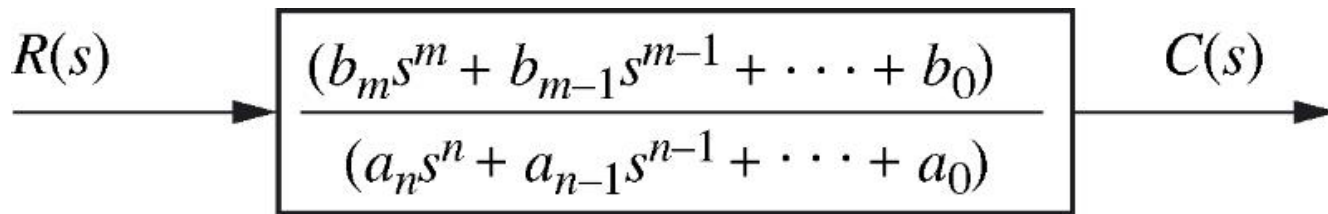

$$\frac{C(s)}{R(s)} = G(s) = \frac{(b_m s^m + b_{m-1} s^{m-1} + \dots + b_0)}{(a_n s^n + a_{n-1} s^{n-1} + \dots + a_0)}$$

# TRANSFER FUNCTIONS OF PHYSICAL SYSTEMS

- **ELECTRICAL NETWORK TRANSFER FUNCTIONS**
- **TRANSLATIONAL MECHANICAL SYSTEM TRANSFER FUNCTIONS**
- **ROTATIONAL MECHANICAL SYSTEM TRANSFER FUNCTIONS**
- **TRANSFER FUNCTIONS FOR SYSTEMS WITH GEARS**
- **ELECTROMECHANICAL SYSTEM TRANSFER FUNCTIONS**
- **ELECTRIC CIRCUIT ANALOGS**



# Basic Elements of Electrical Systems



Symbol →



- The time domain expression relating voltage and current for the **resistor** is given by Ohm's law i-e

$$v_R(t) = i_R(t)R$$

- The Laplace transform of the above equation is

$$V_R(s) = I_R(s)R$$

# Basic Elements of Electrical Systems



- The time domain expression relating voltage and current for the **Capacitor** is given as:

$$v_c(t) = \frac{1}{C} \int i_c(t) dt$$

- The Laplace transform of the above equation (assuming there is no charge stored in the capacitor) is

$$V_c(s) = \frac{1}{Cs} I_c(s)$$

# Basic Elements of Electrical Systems






- The time domain expression relating voltage and current for the **inductor** is given as:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

- The Laplace transform of the above equation (assuming there is no energy stored in inductor) is


$$V_L(s) = LsI_L(s)$$

# V-I and I-V relations

Component	Symbol	V-I Relation	I-V Relation
Resistor		$v_R(t) = i_R(t)R$	$i_R(t) = \frac{v_R(t)}{R}$
Capacitor		$v_c(t) = \frac{1}{C} \int i_c(t) dt$	$i_c(t) = C \frac{dv_c(t)}{dt}$
Inductor		$v_L(t) = L \frac{di_L(t)}{dt}$	$i_L(t) = \frac{1}{L} \int v_L(t) dt$
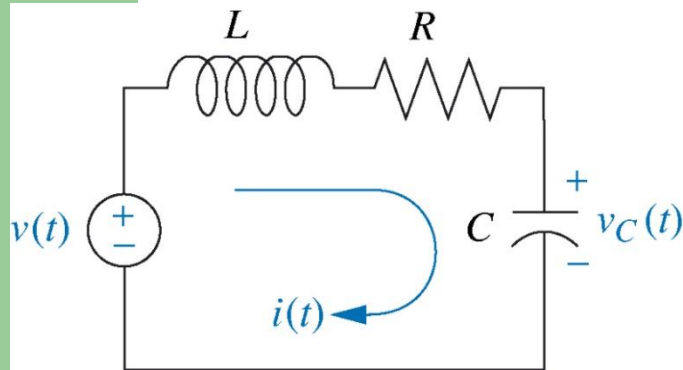
# ELECTRICAL NETWORK TRANSFER FUNCTIONS

Kirchhoff's Voltage Law (KVL), Loop method



$$\sum v_{drop} = 0$$

$$v_L + v_R + v_C - v = 0$$

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

$$i(t) = dq(t)/dt$$

$$L \frac{d^2q(t)}{dt^2} + R \frac{dq(t)}{dt} + \frac{1}{C} q(t) = v(t)$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

$$q(t) = Cv_C(t)$$

$$LC \frac{d^2 v_C(t)}{dt^2} + RC \frac{dv_C(t)}{dt} + v_C(t) = v(t)$$

Laplace transform

$$LC(s^2 V_C(s) - sv_c^0 - \dot{v}_c^0) + RC(sV_C(s) - v_c^0) + V_C(s) = V(s)$$

Zero initial conditions;

$$v_c^0(t=0) = 0; \dot{v}_c^0(t=0) = 0$$

$$(LCs^2 + RCs + 1)V_C(s) = V(s)$$


# ELECTRICAL NETWORK TRANSFER FUNCTIONS

$V_C(s)$  – Output,  $V(s)$  – Input

Transfer function

$$\frac{V_C(s)}{V(s)} = \frac{1}{LCs^2 + RCs + 1}$$
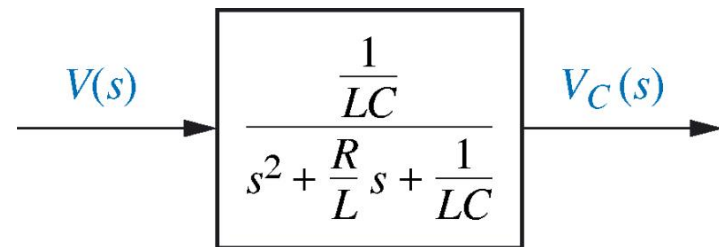
$$\frac{V_C(s)}{V(s)} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$




Block diagram


# ELECTRICAL NETWORK TRANSFER FUNCTIONS

Kirchhoff's Current Law (KCL), Node method


$$\sum_i (i_k)_{in} = 0$$

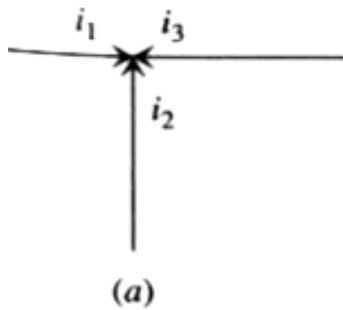

$$i_1 + i_2 + i_3 = 0$$

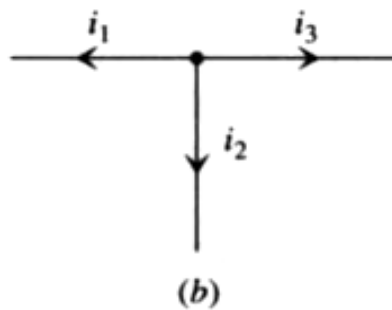

$$-(i_1 + i_2 + i_3) = 0$$

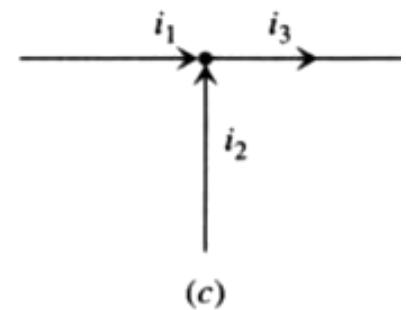

$$i_1 + i_2 - i_3 = 0$$



# ELECTRICAL NETWORK TRANSFER FUNCTIONS

## Impedance Method

$$\frac{V(s)}{I(s)} = Z(s)$$

For the capacitor,

$$V(s) = \frac{1}{Cs} I(s)$$

For the resistor,

$$V(s) = RI(s)$$


For the inductor,

$$V(s) = LsI(s)$$
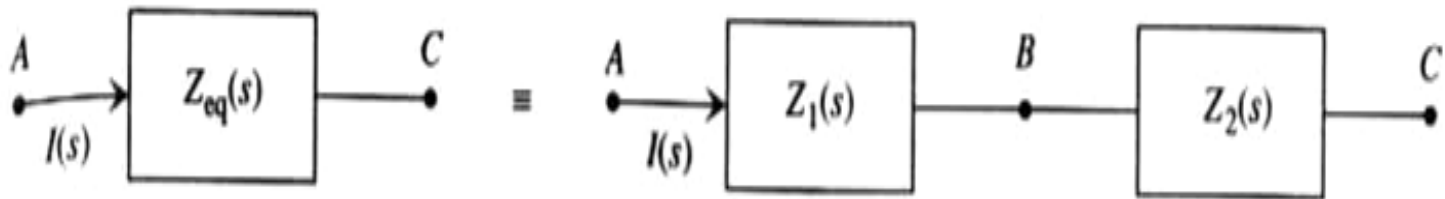
# Elements of Electrical System: Impedance Method

Theorem 1. If there are  $n$  impedance in **series**

$$Z_{eq}(s) = Z_1(s) + Z_2(s) + \dots + Z_n(s)$$



Equivalent impedance for two impedances in series


$$Z_{eq}(s) = Z_1(s) + Z_2(s)$$

# Elements of Electrical System
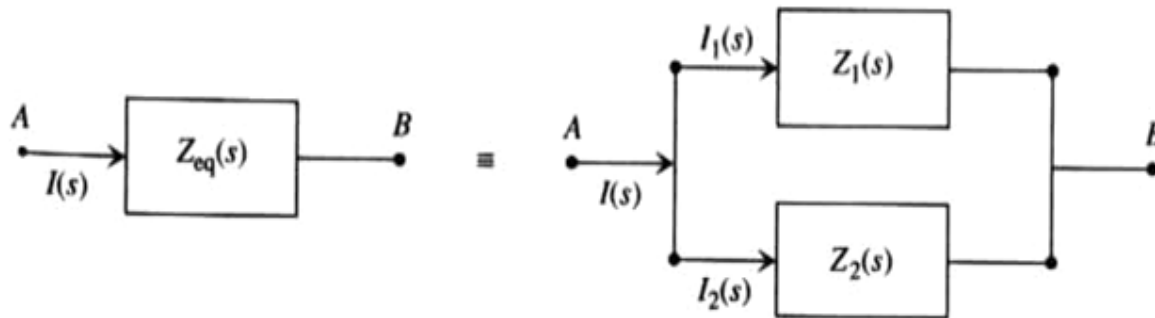
## Impedance Method

Theorem 2. If there are  $n$  impedances in parallel

$$\frac{1}{Z_{eq}(s)} = \frac{1}{Z_1(s)} + \frac{1}{Z_2(s)} + \dots + \frac{1}{Z_n(s)}$$




Equivalent impedance for two impedances in parallel

$$\frac{1}{Z_{eq}(s)} = \frac{1}{Z_1(s)} + \frac{1}{Z_2(s)}$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

Impedance Method

$$\frac{V(s)}{I(s)} = Z(s)$$

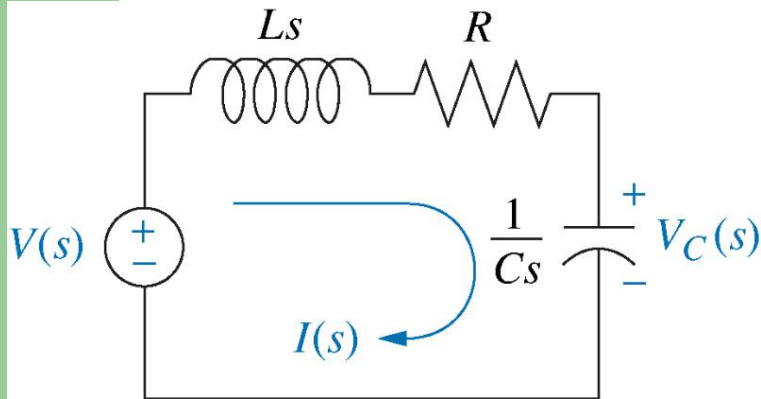

$$\sum v_{drop} = 0$$

$$v_L + v_R + v_C - v = 0$$


$$V_L(s) + V_R(s) + V_C(s) - V(s) = 0$$

$$LsI(s) + RI(s) + V_C(s) - V(s) = 0$$

$$Ls(CsV_C(s)) + R(CsV_C(s)) + V_C(s) - V(s) = 0$$

$$(LCs^2 + RCs + 1)V_C(s) = V(s)$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

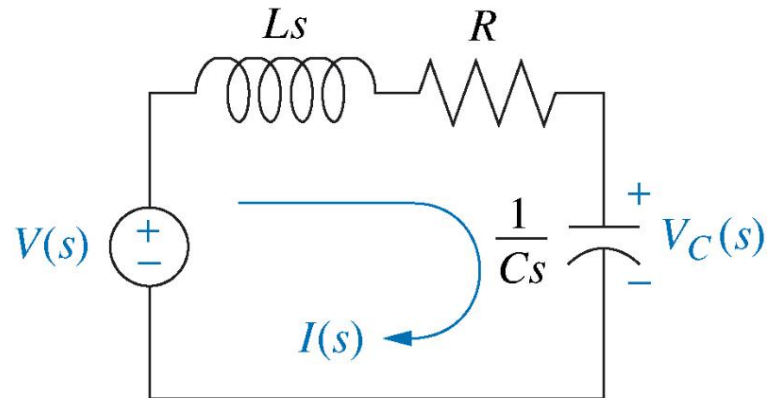


$$(LCs^2 + RCs + 1)V_C(s) = V(s)$$

$$\frac{V_C(s)}{V(s)} = \frac{1}{LCs^2 + RCs + 1}$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

$$\frac{V_C(s)}{V(s)}$$

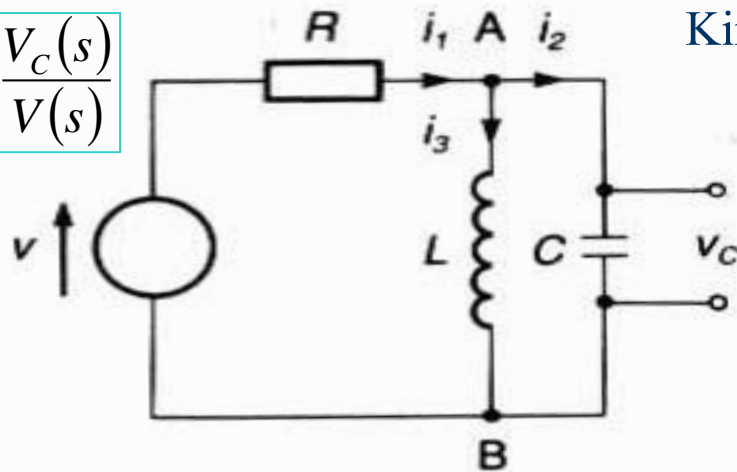

Kirchhoff's Current Law (KCL), Node method

$$\sum_k (i_k)_{in} = 0$$

$$i_1 - i_2 - i_3 = 0 \Leftrightarrow i_2 + i_3 = i_1$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

$$i_1 = \frac{v - v_A}{R}, i_2 = C \frac{dv_A}{dt}, i_3 = \frac{1}{L} \int v_A dt$$

$$i_1 = i_2 + i_3$$



$$\frac{v - v_A}{R} = C \frac{dv_A}{dt} + \frac{1}{L} \int v_A dt$$

$$v_A = v_C$$

$$v = RC \frac{dv_C}{dt} + v_C + \frac{R}{L} \int v_C dt$$

# ELECTRICAL NETWORK TRANSFER FUNCTIONS

Laplace transform with zero initial conditions;



$$V(s) = RCsV_C(s) + V_C(s) + \frac{R}{L} \frac{1}{s} V_C(s)$$

**Transfer function**


$$\frac{V_C(s)}{V(s)} = \frac{Ls}{LRCs^2 + Ls + R}$$



# Divider

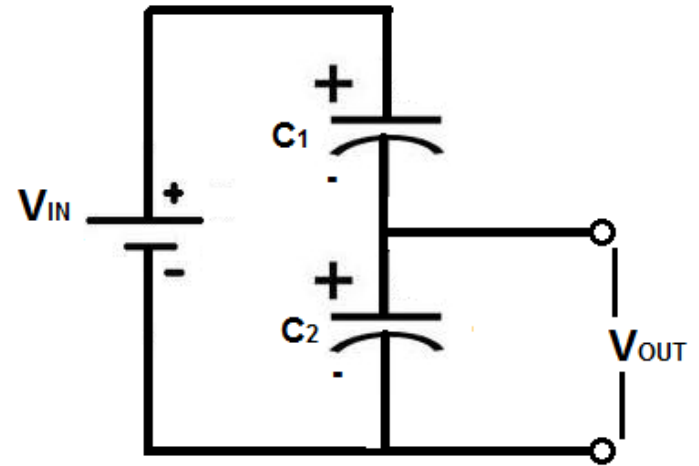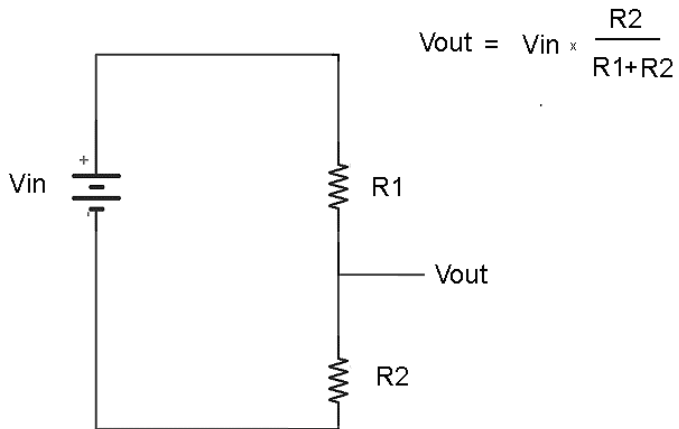



# Filter Circuit

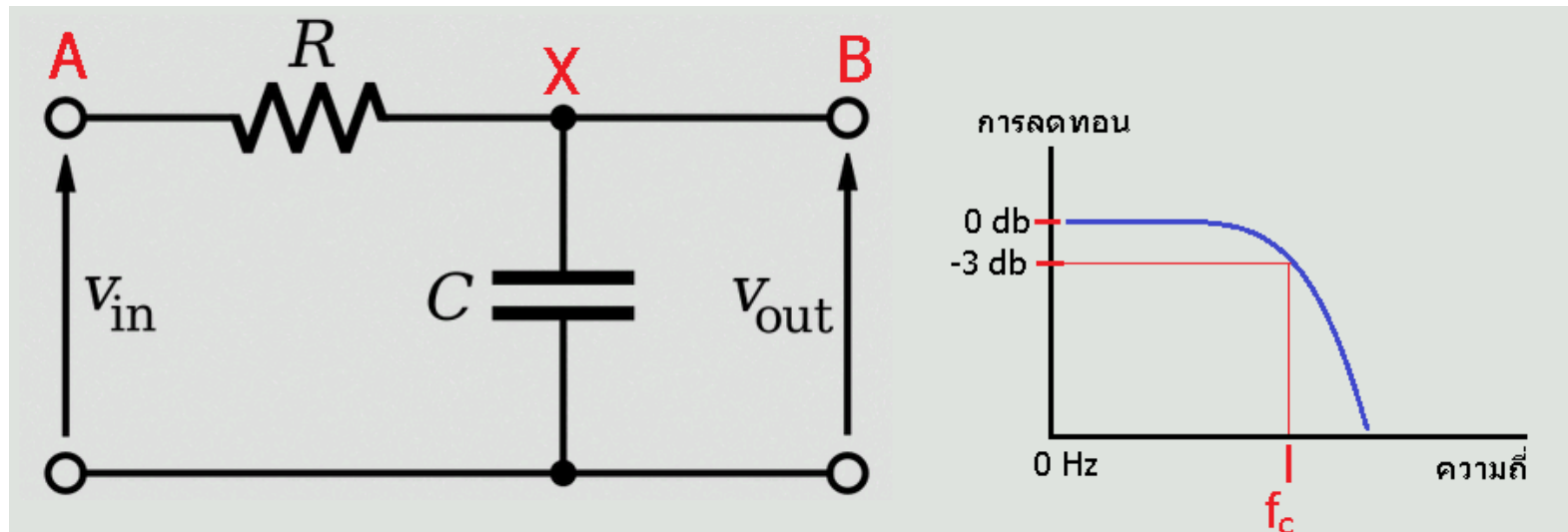


Low-pass Filter

# OPERATIONAL AMPLIFIERS

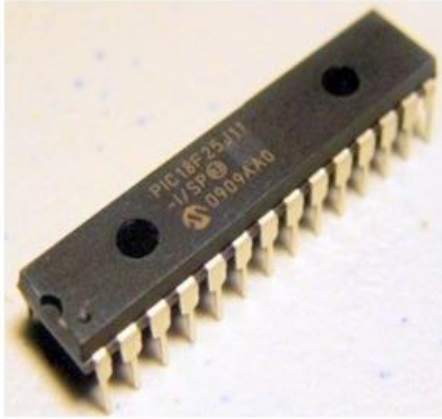Description	PIC18F25J11	PIC24F16KA102
<b>Packaging</b>	28 Pin PDIP 	28 Pin PDIP 
<b>Register</b>	8 Bit	16 Bit
<b>Program Memory</b>	16 KByte	16 KByte
<b>Instruction Clock</b>	4 Cycles	2 Cycles
<b>Price</b>	USD 2.70	USD 2.41
<b>Development Tools</b>	Microchip MPLAB and Microchip C18 or Microchip HI-TECH C for PIC18 C Compiler	Microchip MPLAB and Microchip C30, Microchip HI-TECH C for dsPIC/PIC24 C Compiler
<b>Peripherals</b>	Advance	More Advance
<b>Speed</b>	Up to 12 MIPS at 48 MHz	Up to 16 MIPS at 32 MHz

Microchip PIC18F25J11 and PIC24F16KA102 Microcontroller Basic Comparison


# OPERATIONAL AMPLIFIERS

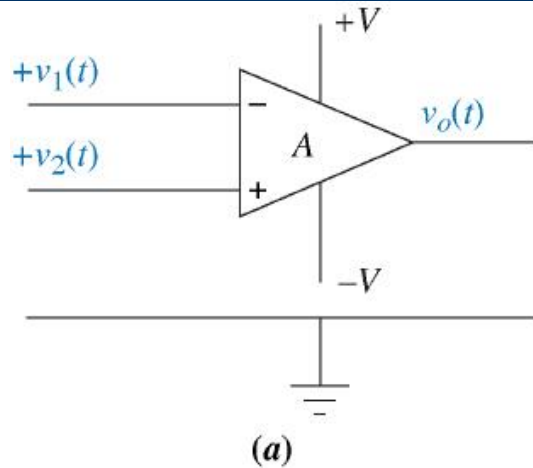


- Inverting Op-Amp
- Non-inverting Op-Amp

1. Differential input,  $v_2(t) - v_1(t)$
2. High input impedance,  $Z_i = \infty$  (ideal)
3. Low output impedance,  $Z_o = 0$  (ideal)
4. High constant gain amplification,  $A = \infty$  (ideal)

# INVERTING OPERATIONAL AMPLIFIERS

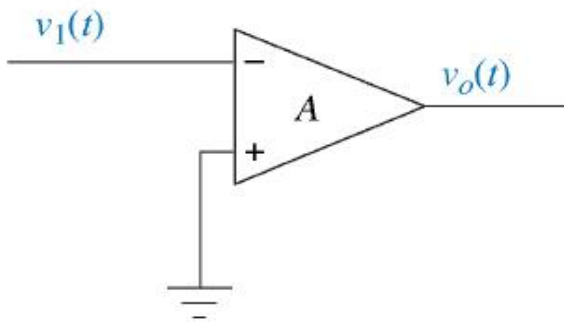

$$v_o(t) = -Av_1(t)$$

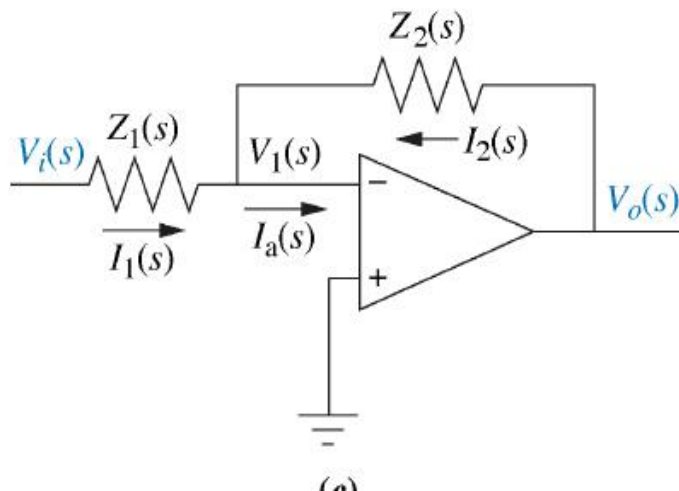

$$I_a(s) = 0$$

$$I_1(s) = -I_2(s)$$

# INVERTING OPERATIONAL AMPLIFIERS


$$I_1(s) = \frac{V_i(s)}{Z_1(s)}$$

$$I_2(s) = \frac{V_o(s)}{Z_2(s)}$$

Transfer function

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$
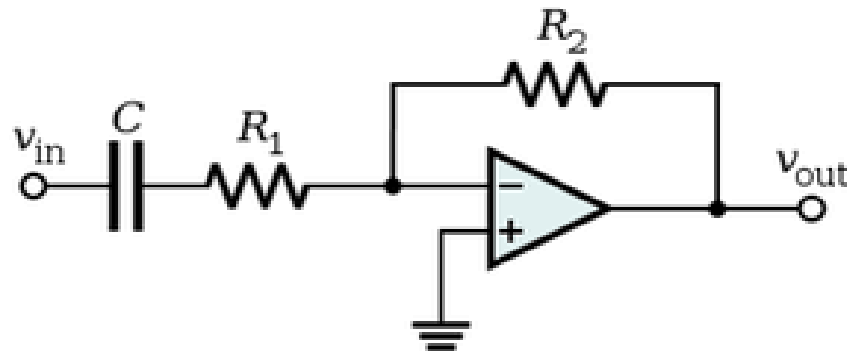
# INVERTING OPERATIONAL AMPLIFIERS: High Pass Filter



High-pass filter circuit

$$Z_{CR_1}(s) = \frac{1}{Cs} + R_1 = \frac{CR_1s + 1}{Cs}$$

$$Z_{R_2}(s) = R_2$$


# INVERTING OPERATIONAL AMPLIFIERS: High Pass Filter

Transfer function


$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{Z_{R_2}(s)}{Z_{CR_1}(s)} = -\frac{R_2}{CR_1s + 1/Cs} = -\frac{CR_2s}{CR_1s + 1}$$


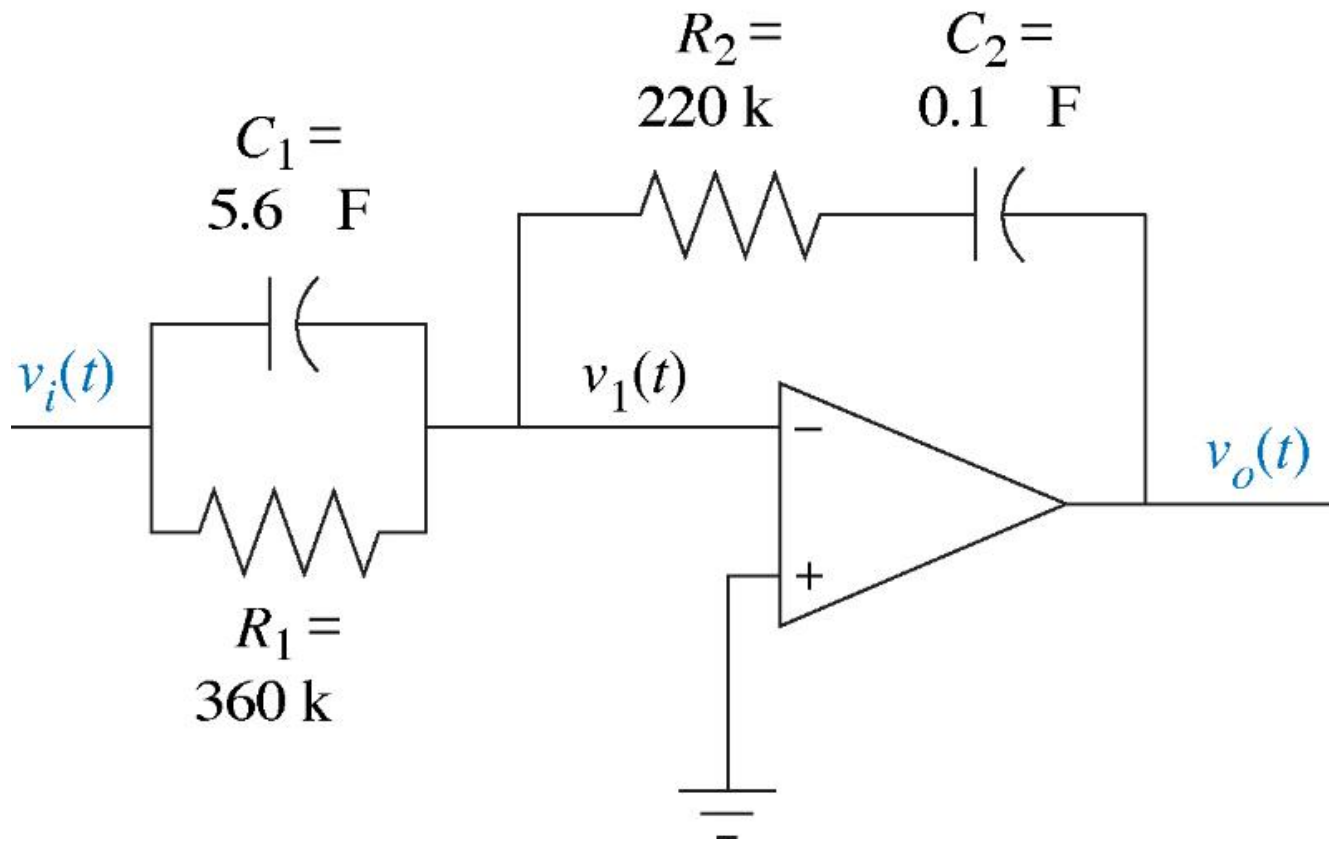
# INVERTING OPERATIONAL AMPLIFIERS: PID Controller


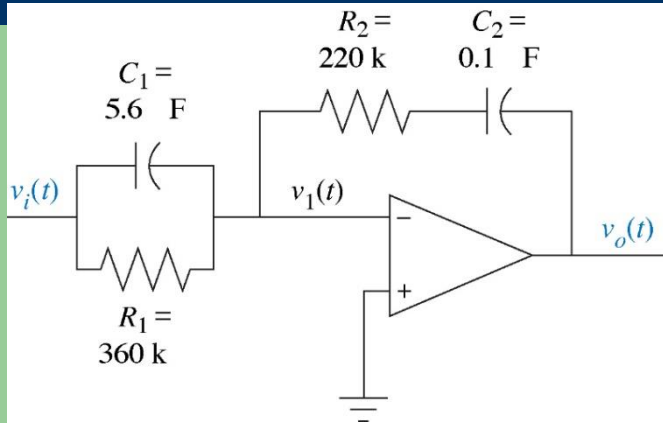
# INVERTING OPERATIONAL AMPLIFIERS: PID Controller




$$\frac{V_o(s)}{V_i(s)} = -1.232 \frac{s^2 + 45.95s + 22.55}{s}$$

$$Z_1(s) = \frac{1}{C_1s + \frac{1}{R_1}} = \frac{1}{5.6 \times 10^{-6}s + \frac{1}{360 \times 10^3}} = \frac{360 \times 10^3}{2.016s + 1} \quad (2.98)$$

$$Z_2(s) = R_2 + \frac{1}{C_2s} = 220 \times 10^3 + \frac{10^7}{s} \quad (2.99)$$

# NON-INVERTING OPERATIONAL AMPLIFIERS

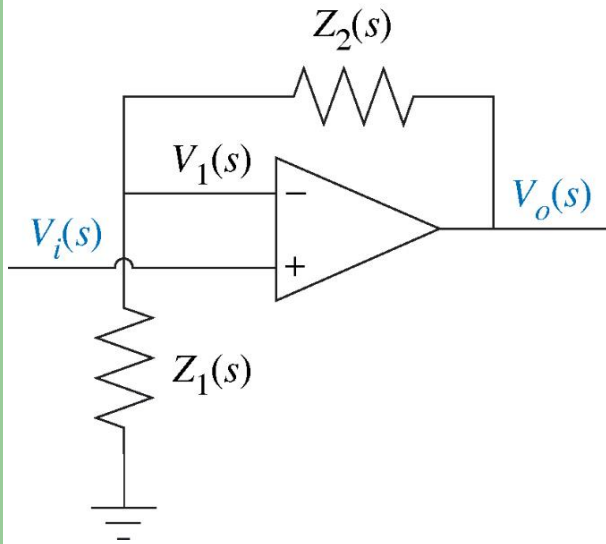

$$V_o(s) = A(V_i(s) - V_1(s))$$


$$V_1(s) = \frac{Z_1(s)}{Z_1(s) + Z_2(s)} V_o(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{A}{1 + AZ_1(s)/(Z_1(s) + Z_2(s))}$$

For large  $A$ , we disregard unity in the denominator

$$\frac{V_o(s)}{V_i(s)} = \frac{Z_1(s) + Z_2(s)}{Z_1(s)}$$

# NON-INVERTING OPERATIONAL AMPLIFIERS

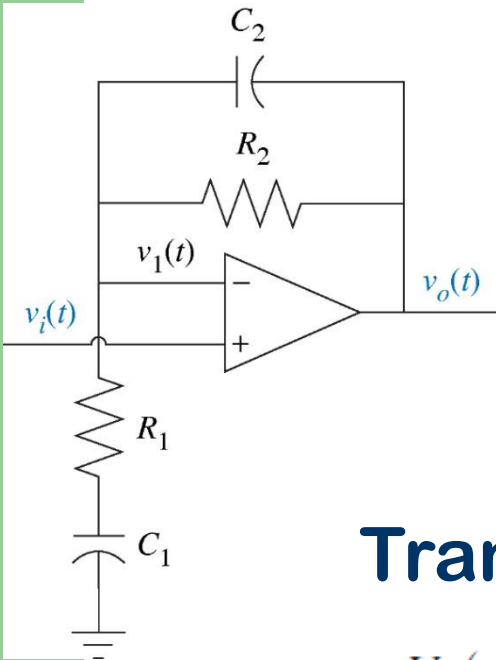

$$Z_1(s) = R_1 + \frac{1}{C_1 s}$$

$$Z_2(s) = \frac{R_2(1/C_2 s)}{R_2 + (1/C_2 s)}$$

## Transfer function

$$\frac{V_o(s)}{V_i(s)} = \frac{C_2 C_1 R_2 R_1 s^2 + (C_2 R_2 + C_1 R_2 + C_1 R_1) s + 1}{C_2 C_1 R_2 R_1 s^2 + (C_2 R_2 + C_1 R_1) s + 1}$$